

# Contents


Preface ix

## Chapter 1 Introduction 02

1-1	The Three Kinds of Formulas	1-4	Current Sources
1-2	Approximations	1-5	Thevenin's Theorem
1-3	Voltage Sources	1-6	Norton's Theorem
		1-7	Troubleshooting

## Chapter 2 Semiconductors 28

2-1	Conductors	2-8	The Unbiased Diode
2-2	Semiconductors	2-9	Forward Bias
2-3	Silicon Crystals	2-10	Reverse Bias
2-4	Intrinsic Semiconductors	2-11	Breakdown
2-5	Two Types of Flow	2-12	Energy Levels
2-6	Doping a Semiconductor	2-13	Barrier Potential and Temperature
2-7	Two Types of Extrinsic Semiconductors	2-14	Reverse-Biased Diode

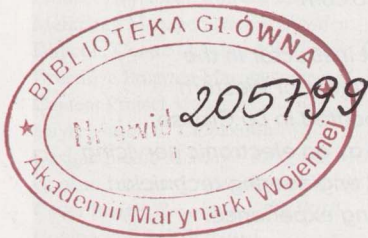

## Chapter 3 Diode Theory 56

3-1	Basic Ideas	3-7	How to Calculate Bulk Resistance
3-2	The Ideal Diode	3-8	DC Resistance of a Diode
3-3	The Second Approximation	3-9	Load Lines
3-4	The Third Approximation	3-10	Surface-Mount Diodes
3-5	Troubleshooting	3-11	Introduction to Electronic Systems
3-6	Reading a Data Sheet		

## Chapter 4 Diode Circuits 86

4-1	The Half-Wave Rectifier	4-7	Peak Inverse Voltage and Surge Current
4-2	The Transformer	4-8	Other Power-Supply Topics
4-3	The Full-Wave Rectifier	4-9	Troubleshooting
4-4	The Bridge Rectifier	4-10	Clippers and Limiters
4-5	The Choke-Input Filter	4-11	Clampers
4-6	The Capacitor-Input Filter	4-12	Voltage Multipliers

## Chapter 5 Special-Purpose Diodes 140

<b>5-1</b>	The Zener Diode	<b>5-7</b>	Load Lines
<b>5-2</b>	The Loaded Zener Regulator	<b>5-8</b>	Light-Emitting Diodes (LEDs)
<b>5-3</b>	Second Approximation of a Zener Diode	<b>5-9</b>	Other Optoelectronic Devices
<b>5-4</b>	Zener Drop-Out Point	<b>5-10</b>	The Schottky Diode
<b>5-5</b>	Reading a Data Sheet	<b>5-11</b>	The Varactor
<b>5-6</b>	Troubleshooting	<b>5-12</b>	Other Diodes

## Chapter 6 BJT Fundamentals 188

<b>6-1</b>	The Unbiased Transistor	<b>6-9</b>	Surface-Mount Transistors
<b>6-2</b>	The Biased Transistor	<b>6-10</b>	Variations in Current Gain
<b>6-3</b>	Transistor Currents	<b>6-11</b>	The Load Line
<b>6-4</b>	The CE Connection	<b>6-12</b>	The Operating Point
<b>6-5</b>	The Base Curve	<b>6-13</b>	Recognizing Saturation
<b>6-6</b>	Collector Curves	<b>6-14</b>	The Transistor Switch
<b>6-7</b>	Transistor Approximations	<b>6-15</b>	Troubleshooting
<b>6-8</b>	Reading Data Sheets		

## Chapter 7 BJT Biasing 240

<b>7-1</b>	Emitter Bias	<b>7-6</b>	Accurate V <sub>BE</sub> Analysis
<b>7-2</b>	LED Drivers	<b>7-7</b>	V <sub>BE</sub> Load Line and Q Point
<b>7-3</b>	Troubleshooting Emitter Bias Circuits	<b>7-8</b>	Two-Supply Emitter Bias
<b>7-4</b>	More Optoelectronic Devices	<b>7-9</b>	Other Types of Bias
<b>7-5</b>	Voltage-Divider Bias	<b>7-10</b>	Troubleshooting V <sub>BE</sub> Circuits
		<b>7-11</b>	PNP Transistors

## Chapter 8 Basic BJT Amplifiers 280

<b>8-1</b>	Base-Biased Amplifier	<b>8-7</b>	Analyzing an Amplifier
<b>8-2</b>	Emitter-Biased Amplifier	<b>8-8</b>	AC Quantities on the Data Sheet
<b>8-3</b>	Small-Signal Operation	<b>8-9</b>	Voltage Gain
<b>8-4</b>	AC Beta	<b>8-10</b>	The Loading Effect of Input Impedance
<b>8-5</b>	AC Resistance of the Emitter Diode	<b>8-11</b>	Swamped Amplifier
<b>8-6</b>	Two Transistor Models	<b>8-12</b>	Troubleshooting

## Chapter 9 Multistage, CC, and CB Amplifiers 326

<b>9-1</b>	Multistage Amplifiers	<b>9-6</b>	Darlington Connections
<b>9-2</b>	Two-Stage Feedback	<b>9-7</b>	Voltage Regulation
<b>9-3</b>	CC Amplifier	<b>9-8</b>	The Common-Base Amplifier
<b>9-4</b>	Output Impedance	<b>9-9</b>	Troubleshooting Multistage Amplifiers
<b>9-5</b>	Cascading CE and CC		

## Chapter 10 Power Amplifiers 366

- |             |                                    |              |                               |
|-------------|------------------------------------|--------------|-------------------------------|
| <b>10-1</b> | Amplifier Terms                    | <b>10-6</b>  | Biasing Class-B/AB Amplifiers |
| <b>10-2</b> | Two Load Lines                     | <b>10-7</b>  | Class-B/AB Driver             |
| <b>10-3</b> | Class-A Operation                  | <b>10-8</b>  | Class-C Operation             |
| <b>10-4</b> | Class-B Operation                  | <b>10-9</b>  | Class-C Formulas              |
| <b>10-5</b> | Class-B Push-Pull Emitter Follower | <b>10-10</b> | Transistor Power Rating       |

## Chapter 11 JFETs 414

- |             |                              |              |                         |
|-------------|------------------------------|--------------|-------------------------|
| <b>11-1</b> | Basic Ideas                  | <b>11-6</b>  | Transconductance        |
| <b>11-2</b> | Drain Curves                 | <b>11-7</b>  | JFET Amplifiers         |
| <b>11-3</b> | The Transconductance Curve   | <b>11-8</b>  | The JFET Analog Switch  |
| <b>11-4</b> | Biasing in the Ohmic Region  | <b>11-9</b>  | Other JFET Applications |
| <b>11-5</b> | Biasing in the Active Region | <b>11-10</b> | Reading Data Sheets     |
|             |                              | <b>11-11</b> | JFET Testing            |

## Chapter 12 MOSFETs 470

- |             |                                  |              |                                |
|-------------|----------------------------------|--------------|--------------------------------|
| <b>12-1</b> | The Depletion-Mode MOSFET        | <b>12-6</b>  | Digital Switching              |
| <b>12-2</b> | D-MOSFET Curves                  | <b>12-7</b>  | CMOS                           |
| <b>12-3</b> | Depletion-Mode MOSFET Amplifiers | <b>12-8</b>  | Power FETs                     |
| <b>12-4</b> | The Enhancement-Mode MOSFET      | <b>12-9</b>  | High-Side MOSFET Load Switches |
| <b>12-5</b> | The Ohmic Region                 | <b>12-10</b> | MOSFET H-Bridge                |
|             |                                  | <b>12-11</b> | E-MOSFET Amplifiers            |
|             |                                  | <b>12-12</b> | MOSFET Testing                 |

## Chapter 13 Thyristors 524

- |             |                                  |             |                          |
|-------------|----------------------------------|-------------|--------------------------|
| <b>13-1</b> | The Four-Layer Diode             | <b>13-5</b> | Bidirectional Thyristors |
| <b>13-2</b> | The Silicon Controlled Rectifier | <b>13-6</b> | IGBTs                    |
| <b>13-3</b> | The SCR Crowbar                  | <b>13-7</b> | Other Thyristors         |
| <b>13-4</b> | SCR Phase Control                | <b>13-8</b> | Troubleshooting          |

## Chapter 14 Frequency Effects 568

- |             |                                    |              |   |
|-------------|------------------------------------|--------------|---|
| <b>14-1</b> | Frequency Response of an Amplifier | <b>14-8</b>  | The Miller Effect                           |
| <b>14-2</b> | Decibel Power Gain                 | <b>14-9</b>  | Risetime-Bandwidth Relationship             |
| <b>14-3</b> | Decibel Voltage Gain               | <b>14-10</b> | Frequency Analysis of BJT Stages            |
| <b>14-4</b> | Impedance Matching                 | <b>14-11</b> | Frequency Analysis of FET Stages            |
| <b>14-5</b> | Decibels above a Reference         | <b>14-12</b> | Frequency Effects of Surface-Mount Circuits |
| <b>14-6</b> | Bode Plots                         |              |   |
| <b>14-7</b> | More Bode Plots                    |              |   |

## Chapter 15 Differential Amplifiers 624

---

- |             |                                    |             |                     |
|-------------|------------------------------------|-------------|---------------------|
| <b>15-1</b> | The Differential Amplifier         | <b>15-5</b> | Common-Mode Gain    |
| <b>15-2</b> | DC Analysis of a Diff Amp          | <b>15-6</b> | Integrated Circuits |
| <b>15-3</b> | AC Analysis of a Diff Amp          | <b>15-7</b> | The Current Mirror  |
| <b>15-4</b> | Input Characteristics of an Op Amp | <b>15-8</b> | The Loaded Diff Amp |

## Chapter 16 Operational Amplifiers 666

---

- |             |                            |             |                                  |
|-------------|----------------------------|-------------|----------------------------------|
| <b>16-1</b> | Introduction to Op Amps    | <b>16-5</b> | Two Op-Amp Applications          |
| <b>16-2</b> | The 741 Op Amp             | <b>16-6</b> | Linear ICs                       |
| <b>16-3</b> | The Inverting Amplifier    | <b>16-7</b> | Op Amps as Surface-Mount Devices |
| <b>16-4</b> | The Noninverting Amplifier |             |                                  |

## Chapter 17 Negative Feedback 710

---

- |             |                                 |             |                    |
|-------------|---------------------------------|-------------|--------------------|
| <b>17-1</b> | Four Types of Negative Feedback | <b>17-4</b> | The ICVS Amplifier |
| <b>17-2</b> | VCVS Voltage Gain               | <b>17-5</b> | The VCIS Amplifier |
| <b>17-3</b> | Other VCVS Equations            | <b>17-6</b> | The ICIS Amplifier |
|             |                                 | <b>17-7</b> | Bandwidth          |

## Chapter 18 Linear Op-Amp Circuit Applications 740

---

- |             |                                 |              |                                    |
|-------------|---------------------------------|--------------|------------------------------------|
| <b>18-1</b> | Inverting-Amplifier Circuits    | <b>18-6</b>  | Summing Amplifier Circuits         |
| <b>18-2</b> | Noninverting-Amplifier Circuits | <b>18-7</b>  | Current Boosters                   |
| <b>18-3</b> | Inverter/Noninverter Circuits   | <b>18-8</b>  | Voltage-Controlled Current Sources |
| <b>18-4</b> | Differential Amplifiers         | <b>18-9</b>  | Automatic Gain Control             |
| <b>18-5</b> | Instrumentation Amplifiers      | <b>18-10</b> | Single-Supply Operation            |

## Chapter 19 Active Filters 788

---

- |             |   |              |  |
|-------------|---|--------------|--|
| <b>19-1</b> | Ideal Responses                               | <b>19-7</b>  | VCVS Equal-Component Low-Pass Filters  |
| <b>19-2</b> | Approximate Responses                         | <b>19-8</b>  | VCVS High-Pass Filters                 |
| <b>19-3</b> | Passive Filters                               | <b>19-9</b>  | MFB Bandpass Filters                   |
| <b>19-4</b> | First-Order Stages                            | <b>19-10</b> | Bandstop Filters                       |
| <b>19-5</b> | VCVS Unity-Gain Second-Order Low-Pass Filters | <b>19-11</b> | The All-Pass Filter                    |
| <b>19-6</b> | Higher-Order Filters                          | <b>19-12</b> | Biquadratic and State-Variable Filters |

# Chapter 20 Nonlinear Op-Amp Circuit Applications 850

<b>20-1</b>	Comparators with Zero Reference	<b>20-6</b>	Waveform Conversion
<b>20-2</b>	Comparators with Nonzero References	<b>20-7</b>	Waveform Generation
<b>20-3</b>	Comparators with Hysteresis	<b>20-8</b>	Another Triangular Generator
<b>20-4</b>	Window Comparator	<b>20-9</b>	Active-Diode Circuits
<b>20-5</b>	The Integrator	<b>20-10</b>	The Differentiator
		<b>20-11</b>	Class-D Amplifier

# Chapter 21 Oscillators 902

<b>21-1</b>	Theory of Sinusoidal Oscillation	<b>21-7</b>	The 555 Timer
<b>21-2</b>	The Wien-Bridge Oscillator	<b>21-8</b>	Astable Operation of the 555 Timer
<b>21-3</b>	Other RC Oscillators	<b>21-9</b>	555 Circuit Applications
<b>21-4</b>	The Colpitts Oscillator	<b>21-10</b>	The Phase-Locked Loop
<b>21-5</b>	Other LC Oscillators	<b>21-11</b>	Function Generator ICs
<b>21-6</b>	Quartz Crystals		

# Chapter 22 Regulated Power Supplies 958

<b>22-1</b>	Supply Characteristics	<b>22-5</b>	Current Boosters
<b>22-2</b>	Shunt Regulators	<b>22-6</b>	DC-to-DC Converters
<b>22-3</b>	Series Regulators	<b>22-7</b>	Switching Regulators
<b>22-4</b>	Monolithic Linear Regulators		

<b>Appendix A</b>	Data Sheet List 1010
<b>Appendix B</b>	Mathematical Derivations 1011
<b>Appendix C</b>	Multisim Primer 1017
<b>Appendix D</b>	Thevenizing the R/2R D/A Converter 1063
<b>Appendix E</b>	Summary Table Listing 1065
<b>Appendix F</b>	Digital/Analog Trainer System 1067
<b>Glossary</b>	1070
<b>Answers</b>	Odd-Numbered Problems 1083
<b>Index</b>	1089