



CONTENTS

	PAGE
<b>II Electrical Effects and Units—continued</b>	
17.5. Self-Capacity of Coils . . . . .	50
17.6. Miscellaneous Inductance Formulae . . . . .	51
18. Magneto-motive Force = m.m.f. . . . .	57
19. Reluctance of a Magnetic Circuit . . . . .	57
20. Permeability . . . . .	58
21. Capacity (Capacitance) . . . . .	58
22. Definition of the Practical Units of Capacity: the Farad, the Microfarad and the Micro-Microfarad . . . . .	59
22.1. Capacity Formulae . . . . .	59
23. Dielectric Constant . . . . .	60
23.1. Dielectric Constants . . . . .	61
23.2. Characteristics of Shell KB30 Transformer Oil . . . . .	61
24. Electrolytic Condensers . . . . .	61
25. Interaction between Magnetic Field and Current . . . . .	64
26. Lenz's Law and its Inverse . . . . .	65
27. Thermo-electric Effect . . . . .	65
28. Contact Potentials . . . . .	65
29. "Dry" and "Wet" Contacts . . . . .	65
30. Conversion Tables between Units . . . . .	66
31. Voltage Breakdown in Air . . . . .	76
31.1. Use of Spark Gaps as Voltage Limiters . . . . .	78
31.2. Procedure when a Flashover Occurs . . . . .	78
31.3. Causes of Flashover . . . . .	79
32. Other Physical Effects . . . . .	79
33. Mass and Weight . . . . .	80
34. Density and Specific Gravity . . . . .	80
35. Relations between Different Kinds of Energy . . . . .	81
36. Current-carrying Capacity of Conductors . . . . .	83
99. Numerical Examples . . . . .	84
<b>III The Sine Wave and Vectors</b>	89
1. Trigonometrical Definitions . . . . .	89
2. Form of a Sine Wave . . . . .	92
3. Representation of Sine Waves by Vectors . . . . .	95
3.1. Addition of Vectors . . . . .	97
3.2. Derivation of Formulae for the Addition of Sine Waves and Vectors . . . . .	98
4. The Complex Plane . . . . .	100
5. Representation of the Angle of a Vector by $e^{j\theta}$ . . . . .	104
6. Negative Vectors and Negative Angles . . . . .	105
7. Cosine Waves . . . . .	106
99. Numerical Examples . . . . .	106
<b>IV Relations between Steady Voltages and Direct Currents</b>	110
1. Resistance and Conductivity . . . . .	110
2. Internal Electromotive Force in Generators . . . . .	110
3. Resistances in Series . . . . .	111
4. Resistances in Parallel . . . . .	112
5. Back Electromotive Force . . . . .	113
6. Power in Direct-Current Circuits . . . . .	113
6.1. Energy Stored in a Condenser . . . . .	114
6.2. Energy Stored in an Inductance . . . . .	114
7. Time Constants . . . . .	115
99. Numerical Examples . . . . .	118

CONTENTS

	PAGE
<b>V Relations between Alternating Voltages and Currents</b>	120
1. Relation between Voltage across a Resistance, and Current . . . . .	120
2. Relation between Voltage across an Inductance, and Current . . . . .	120
3. Relation between Voltage across a Capacity, and Current . . . . .	122
4. Impedance and Complex Quantities . . . . .	123
5. Addition and Subtraction of Complex Quantities . . . . .	127
6. Multiplication of Complex Quantities . . . . .	128
7. Division of Complex Quantities . . . . .	128
8. Impedances in Series . . . . .	129
9. Condensers in Series . . . . .	129
10. Impedances in Parallel . . . . .	130
11. Admittance . . . . .	133
12. Vector and Scalar Notation and Mixed Notation . . . . .	133
13. The Principle of Superposition . . . . .	135
14. Reciprocity Theorem . . . . .	136
15. Thévenin's Theorem . . . . .	136
16. Parallel Representation of Impedances . . . . .	137
17. Reactance Chart . . . . .	140
18. Kirchhoff's Laws . . . . .	142
19. Impedance Potentiometers . . . . .	145
99. Numerical Examples . . . . .	147
<b>VI Selective Circuits: Resonance and Tuning</b>	154
1. Series Resonance . . . . .	155
2. Parallel Resonance . . . . .	157
2.1. Condition at Parallel Resonance . . . . .	158
2.1.1. Relation between $f_r$ and $f_0$ . . . . .	160
2.2. Conditions for Maximum Impedance of a Parallel Resonant Circuit . . . . .	160
2.3. Natural Frequency . . . . .	161
2.4. Practical Application of Parallel Resonant Circuit . . . . .	161
2.5. Selectivity and Response . . . . .	162
2.6. Choice of Values of Elements in Tuned Circuits . . . . .	164
3. Rejector and Acceptor Circuits . . . . .	165
4. Other Types of Selective Circuits . . . . .	166
5. Decay Factor, Decay Index, Decrement, $Q$ and Natural Frequency of a Circuit . . . . .	166
5.1. Definitions . . . . .	167
5.2. Measurement of $Q$ , Decrement, Decay Factor and Decay Index of a Coil . . . . .	167
99. Numerical Examples . . . . .	172
<b>VII Power in Alternating Current Circuits</b>	177
1. Power delivered to a Resistance by a Sinusoidal Alternating Current . . . . .	177
2. R.M.S. Sum of a Number of Alternating Currents or Voltages . . . . .	177
3. Power in Circuits containing both Reactance and Resistance . . . . .	178
4. Power Factor . . . . .	179
5. Power Ratios: The Decibel . . . . .	179

CONTENTS

	PAGE
<b>VII Power in Alternating Current Circuits—continued</b>	
6. Level and Volume . . . . .	181
6.1. Level of Tone . . . . .	181
6.2. The Nature of Programme and Noise . . . . .	183
6.3. Volume of Programme and Noise . . . . .	184
6.4. Applications . . . . .	186
7. Levels in Speech and Music Circuits . . . . .	187
8. Level of Line-Up Tone and Use of Line-Up Tone . . . . .	187
9. Impedance Matching . . . . .	188
10. Reflection Loss . . . . .	190
10.1. Transition Loss . . . . .	191
11. Use of Impedance Transforming Circuits to avoid Reflection Loss . . . . .	192
12. Insertion Loss and Gain . . . . .	195
13. Coupled Circuits and Coupling Factor . . . . .	196
13.1. Leakage Flux . . . . .	196
13.2. Coupling Factor . . . . .	197
13.3. Mutual Inductance . . . . .	198
13.4. Leakage Inductance . . . . .	198
13.5. Impedance looking into Primary of Coupled Circuit . . . . .	198
13.6. Mutual Impedance . . . . .	199
13.7. Adjustment of Coupling . . . . .	199
14. Design of Impedance Matching or Coupling Circuits . . . . .	201
14.1. kVA to Kilowatts Ratio . . . . .	201
14.2. Current per Kilowatt through Inductances . . . . .	202
14.3. Design of Coupling Circuits in which the kVA/kW Ratio does not have to be considered . . . . .	204
14.3.1. Broad-Band Amplifiers . . . . .	211
14.3.2. Tuned Amplifiers (Narrow-Band Amplifiers) . . . . .	213
14.4. Method of Adjusting and Tuning Coupled Circuits . . . . .	213
14.5. Design of Coupling Circuits in which the kVA/kW Ratio has to be taken into Account . . . . .	215
14.6. Design of Coupling Circuits without the use of Charts . . . . .	216
15. Effective Inductance of two Inductances $L_1$ and $L_2$ with Mutual Coupling $M$ between them . . . . .	217
16. Measurement of Coupling Factor $k$ of two Inductances . . . . .	219
17. Attenuators . . . . .	220
17.1. Attenuators in which $Z_1$ and $Z_2$ are unequal: Dissymmetrical $T$ and $\pi$ Networks . . . . .	221
99. Numerical Examples . . . . .	221
<b>VIII Harmonic Analysis and Distortion</b> . . . . .	229
1. Periodic Waves . . . . .	229
1.1. Spectra of Amplitude Modulated Waves . . . . .	238
2. Spectrum of Speech and Music . . . . .	242
3. Distortion . . . . .	247
3.1. Response Distortion: Response Characteristics . . . . .	247
3.1.1. Permissible Deviation of Response Characteristics in Audio-Frequency Circuits . . . . .	249
3.2. Phase Distortion in Audio-Frequency Circuits . . . . .	251
3.3. Non-Linear Distortion . . . . .	256
4. Effects of Distortion in Radio-Frequency Circuits . . . . .	258
4.1. Measurement of Distortion in Radio-Frequency Circuits . . . . .	259
4.2. Effect of Attenuation and Phase Shift of Sidebands . . . . .	259

CONTENTS

	PAGE
<b>IX Thermionic Valves</b>	263
1. The Diode . . . . .	263
2. The Triode . . . . .	265
3. Anode Impedance = $R_0$ . . . . .	266
4. Load Line . . . . .	268
4.1. Use of the Load Line . . . . .	270
4.2. Grid Bias and Cut-Off . . . . .	272
5. Voltage Amplification . . . . .	272
6. Voltage Amplification Factor of Valve = $\mu$ . . . . .	274
7. Mutual Conductance of Valve = $g_m$ . . . . .	275
7.1. Relation between $g_m$ , $\mu$ and $R_0$ . . . . .	275
8. Power Amplification . . . . .	276
9. Non-Linearity . . . . .	276
10. Capacities in a Triode . . . . .	277
11. The Screen-Grid Valve or Tetrode . . . . .	278
11.1. Secondary Emission . . . . .	278
12. The Pentode . . . . .	279
13. Mixers . . . . .	281
13.1. Hexode . . . . .	281
13.2. Heptode . . . . .	282
13.3. Octode . . . . .	282
14. Variable $\mu$ Valves . . . . .	282
15. Composite Valves . . . . .	283
16. Short-Wave Valves . . . . .	283
17. Anode Dissipation . . . . .	284
17.1. Air-Cooled Anodes . . . . .	284
17.2. Water-Cooled Anodes . . . . .	284
17.3. Cooling of Seals . . . . .	285
18. Operation and Maintenance of Thermionic Valves . . . . .	285
18.1. Procedure for Applying Supplies to a Valve . . . . .	285
18.2. Marked Volts (Filament Volts) . . . . .	286
18.3. New Valves (Introduction into service of) . . . . .	288
18.4. Gas Test . . . . .	288
18.4.1. Pirani Test . . . . .	289
18.5. Service Test on Spare Valves . . . . .	289
18.6. Emission Tests . . . . .	289
18.6.1. Total Emission Test . . . . .	289
18.6.2. Suppressed Emission Test . . . . .	289
18.6.3. Emission Tests on Medium-Size Valves and Small Valves . . . . .	290
18.7. Valve Cooling Water . . . . .	290
19. Total Emission, Peak Emission, Peak Anode Current, and Cathode Emission . . . . .	290
20. Grid Input Impedance of Valves . . . . .	292
<b>X Amplifiers</b>	293
1. Class A Amplifiers . . . . .	293
1.1. Phase Relation between Grid Volts and Anode Volts . . . . .	296
2. Resistance-Coupled Amplifier . . . . .	297
3. Choke-Coupled Amplifier . . . . .	298
4. Load Line for Resistance-Coupled Amplifier . . . . .	298
5. Load Line for Choke-Coupled Amplifier . . . . .	299
6. Transformer-Coupled Amplifier . . . . .	300
7. Automatic Grid Bias . . . . .	302

CONTENTS

	PAGE
<b>X Amplifiers—continued</b>	
8. Push-Pull Connection of Valves . . . . .	303
9. Class B Amplifiers . . . . .	306
10. Design of Push-Pull Output Transformers for Class A and Class B Amplifiers . . . . .	307
11. Power Output and Efficiency of Class B Amplifiers . . . . .	308
11.1. Comparison of Power Output of Class A and Class B Amplifiers : Adjustment of Load Line for Maximum Output . . . . .	310
12. Variation of Power Consumption of Anode Circuit of Amplifier as Grid Drive Varies . . . . .	316
13. Variation of Anode Dissipation as Grid Drive Varies . . . . .	317
14. Theoretical Optimum Value of Anode Load Impedance . . . . .	317
15. Tuned Amplifiers . . . . .	319
16. Definitions of A, B, and C Tuned Amplifiers . . . . .	321
17. Circuit Arrangement of Tuned Amplifiers . . . . .	322
18. Make-up Current . . . . .	324
19. Neutralization of Anode-Grid Capacity of Valves . . . . .	324
19.1. Circuits which Provide Stability and Freedom from Feedback . . . . .	325
19.1.1. The Split Anode Neut Circuit . . . . .	325
19.1.2. Push-Pull Neut Circuit . . . . .	327
19.1.3. Inductance-Capacity Potentiometer Neut Circuit . . . . .	329
19.2. The Split-Grid Neut Circuit . . . . .	330
19.3. Neut Circuit in High-Power Tetrodes . . . . .	332
20. Adjustment of Neut Condensers . . . . .	333
20.1. Method I. Direct Adjustment of Loss . . . . .	333
20.2. Method II. Grid Current Method . . . . .	334
20.3. Method III. Anode-Current Grid-Current Method . . . . .	335
20.4. Method IV. Anode Current Method . . . . .	336
20.5. Method of Neuting to Use . . . . .	336
20.6. Neuting of Short-Wave Amplifiers . . . . .	338
21. Design of Class A Tuned Amplifiers . . . . .	338
22. Class B and C Tuned Amplifiers . . . . .	338
22.1. Definition of Angle of Current Flow . . . . .	340
22.2. Relation between Angle of Current Flow and Anode Current Ratios: Peak Fundamental to Peak, Peak Fundamental to Mean, and Mean to Peak Ratio . . . . .	340
22.3. Relation between Load Line in Class C Amplifier and Impedance Facing Anode . . . . .	343
23. Power Output of a Class C Tuned Amplifier . . . . .	344
23.1. Power Output of a Class B Amplifier . . . . .	345
24. Anode Efficiency of a Class C Tuned Amplifier . . . . .	345
24.1. Anode Efficiency of a Class B Amplifier (See also X:30) . . . . .	345
24.2. Anode Efficiency of a Class B Tuned Amplifier Transmitting a Modulated Wave . . . . .	345
25. The Angle of Current Flow . . . . .	346
25.1. Determination of $\theta$ , the Angle of Current Flow . . . . .	346
25.2. Effect of Changing the Angle of Current Flow, $\theta$ . . . . .	349
25.2.1. Comparison of Performance of Class B and Class C Tuned Amplifiers (Relation between Angle of Current Flow, Grid Peak Volts, Effective Grid Peak Volts, Working Bias and Cut-off Bias) . . . . .	351

CONTENTS

	PAGE
<b>X Amplifiers—continued</b>	
25.2. Detailed Examination of the Effect of Changing the Angle of Current Flow in a Class C Amplifier . . . . .	355
25.3. Choice of Angle of Current Flow . . . . .	357
25.4. Determination of Grid Bias and Grid Drive to Produce a Required Angle of Current Flow . . . . .	358
26. Practical Design of a Class C Amplifier . . . . .	359
26.1. Grid Loading of Linear Class B Amplifiers . . . . .	362
26.2. Choice of Valve for use in Class C Amplifiers . . . . .	363
26.3. Determination of Working Conditions of a Class C Amplifier which is not driven into Anode Limitation . . . . .	366
26.3.1. Determination of Anode Load Impedance . . . . .	367
27. Anode Limitation . . . . .	368
27.1. Asymptote . . . . .	375
28. Variation of Anode Current as Anode Circuit is Tuned . . . . .	375
29. Variation of Grid Current as Anode Circuit is Tuned . . . . .	376
30. Working Conditions of Class B Tuned Amplifier taking into account No-Drive Standing Feed . . . . .	376
31. Examination of a Practical Tuned Amplifier . . . . .	379
32. Design of Output Coupling Circuit for a Push-Pull Class B or C Tuned Amplifier . . . . .	382
33. Practical Measurement of Valve Anode Efficiency . . . . .	383
33.1. Measurement of Valve Anode Efficiency by Temperature Rise of Anode Cooling Water . . . . .	384
34. Anode Peak Volts and Anode Peak Current in a Modulated Amplifier or other Amplifier driven into Anode Limitation . . . . .	386
35. Inverted Amplifier . . . . .	387
35.1. Necessity for Modulating the Drive Stage . . . . .	390
35.2. Summary . . . . .	391
35.3. Circuit of Practical Inverted Amplifier and Driver . . . . .	391
35.4. Design of Inverted Amplifier and Driver Stage . . . . .	392
35.5. Relations in a Class A Inverted Amplifier . . . . .	395
35.6. Relations in a Class C Inverted Amplifier . . . . .	396
35.6.1. Power Output from an Inverted Amplifier . . . . .	397
35.6.2. Power Amplification of an Inverted Amplifier . . . . .	397
35.6.3. Percentage Modulation Realizable with an Inverted Amplifier . . . . .	398
35.7. Operation and Adjustment of Inverted Amplifiers . . . . .	398
36. Short-Wave Amplifiers . . . . .	399
37. Valve Anode Efficiency, Valve Anode Circuit Efficiency and Output Efficiency of an Amplifying Stage . . . . .	399
38. Grid Dissipation in a Class C Amplifier . . . . .	401
39. D.C. Amplifiers . . . . .	402
99. Examples . . . . .	405
<b>XI Oscillators</b>	412
1. Early Views on Oscillators . . . . .	412
1.1. Standard Oscillator Circuits . . . . .	416
1.2. Frequency Stabilization of Oscillators . . . . .	417
2. Present Views on Oscillators . . . . .	421
2.1. Series Resonance Oscillator . . . . .	421
3. Design and Performance of a Practical Oscillator . . . . .	425

CONTENTS

	PAGE
<b>XI Oscillators—continued</b>	
4. Crystal Oscillators . . . . .	428
4.1. The $A_T$ Cut Plate . . . . .	431
4.2. Frequency Stability of Crystal Oscillators using $A_T$ Cut Plates . . . . .	433
4.3. Crystal Oscillator Circuits . . . . .	433
4.3.1. Series Resonance Type . . . . .	433
4.3.2. The Meecham Crystal Bridge Oscillator Circuit . . . . .	434
4.3.3. Miller Circuit Crystal Oscillator . . . . .	435
4.4. Crystal Ovens . . . . .	437
5. Dynatron Oscillators . . . . .	439
6. The Two Types of Negative Resistance . . . . .	440
7. Resonant Line Oscillators . . . . .	440
8. Electron-Coupled Oscillator . . . . .	443
9. Beat Oscillators . . . . .	444
9.1. Intermodulation of Two Frequencies in a Square Law Modulator . . . . .	444
9.2. Frequency Stability of Beat Oscillators . . . . .	446
10. Resistance-Capacity Oscillator . . . . .	447
11. Freak Oscillations . . . . .	449
12. Parasitic Oscillations . . . . .	450
12.1. Detection of Parasitic Oscillations . . . . .	450
12.2. Causes of Parasitic Oscillation—particularly affecting Audio-Frequency Amplifiers . . . . .	451
12.3. Causes of Parasitic Oscillations—particularly affecting Radio-Frequency Amplifiers . . . . .	454
12.4. Location of Parasitic Oscillations . . . . .	459
12.4.1. Inter-stage Oscillations . . . . .	460
12.4.2. Oscillations involving Input and output Lines . . . . .	461
12.4.3. Oscillations Internal to Stage . . . . .	462
12.4.4. Oscillations in R.F. Amplifiers . . . . .	462
13. Stability Tests on Transmitters . . . . .	463
<b>XII Drive Equipment</b>	465
1. Definition of Drive Equipment . . . . .	465
2. Cairo Requirements on Frequency Stability of Transmitters . . . . .	465
3. Synchronized Operation of Transmitters on the same Wavelength . . . . .	465
4. The Beat Indicator . . . . .	467
5. Methods of Frequency Checking and Adjustment in Synchronized Groups . . . . .	469
5.1. Frequency Checking by Radio . . . . .	469
5.2. Frequency Checking By Line . . . . .	470
6. Frequency Dividers . . . . .	470
6.1. Locked Oscillators . . . . .	470
6.2. Multivibrators . . . . .	471
6.2.1. Single-Circuit Divider . . . . .	475
6.2.1.1. Method of Operation . . . . .	476
6.2.2. Locking of Multivibrators . . . . .	478
6.2.2.1. Locking Condition for Division by an Odd Number . . . . .	479
6.2.2.2. Locking Condition for Division by an Even Number . . . . .	480
6.2.2.3. Adjustment of Relative Lengths of the Two Half-Periods of a Multivibrator . . . . .	481
6.3. Modulator Dividers . . . . .	482

CONTENTS

	PAGE
<b>XII Drive Equipment—continued</b>	
7. Frequency Multipliers . . . . .	486
7.1. Harmonic-Generator Multiplier . . . . .	488
7.2. Harmonic Generators for Multiplying by Odd Numbers . . . . .	489
7.3. Harmonic Generators for Multiplying by Even Numbers . . . . .	489
7.4. Limitation on Multiplication Factor . . . . .	491
8. Vernier Scales . . . . .	494
<b>XIII Modulators and Modulation</b>	496
1. Different Types of Modulation . . . . .	496
2. Heising or Choke Modulation . . . . .	499
3. Class B Modulation . . . . .	501
3.1. Temporary Conversion of Class B Modulator to Class A Operation . . . . .	502
3.2. Series Modulation . . . . .	503
3.3. Design of a Series Modulator . . . . .	506
4. Principle of a Modulated Amplifier . . . . .	507
4.1. Upward and Downward Modulation in Modulated Amplifiers . . . . .	514
4.2. Initial Adjustment of a Modulated Amplifier . . . . .	515
4.3. Simple Procedure for adjusting a Modulated Amplifier . . . . .	520
4.4. Power Handling Capacity . . . . .	523
5. Diode Modulator . . . . .	524
6. Class C Grid Modulator . . . . .	526
7. Anode Bend Modulator . . . . .	530
8. Suppressor Grid Class C Modulator . . . . .	533
8.1. Anode Modulation of Pentode (Suppressor Grid Modulator) . . . . .	536
9. Conversion to 100% Modulation . . . . .	536
10. Push-Pull or Balanced Modulators . . . . .	537
10.1. Double Balanced Modulator . . . . .	539
10.2. Use of Tetrodes in Modulated Amplifier . . . . .	542
11. Spectrum of Modulated Wave . . . . .	542
11.1. Amplitude-Modulated Wave . . . . .	542
11.2. Phase-Modulated Wave . . . . .	546
11.3. Frequency-Modulated Wave . . . . .	547
11.4. Modulation by a Band of Frequencies . . . . .	548
11.5. Numerical Determination of Spectra of Frequency-Modulated and Phase-Modulated Waves . . . . .	549
11.6. Frequency Range occupied by a Frequency-Modulated or a Phase-Modulated Wave . . . . .	555
11.7. Reduction of Noise Level at the Receiver in a Frequency-Modulation System . . . . .	556
11.7.1. Behaviour of the Limiter . . . . .	557
11.7.2. Demonstration that the Effective Noise Level in the Receiver is inversely proportional to the Amplitude of Carrier Frequency Swing . . . . .	557
11.7.3. Comparison of Speech-to-Noise Ratios in Amplitude-Modulated and Frequency-Modulated Systems . . . . .	559
11.8. False Phase Modulation . . . . .	561
12. Heising Modulation Formulae . . . . .	561

CONTENTS

	PAGE
<b>XIV Transmitter Types</b>	<b>566</b>
1. Trend of Development . . . . .	566
2. Low-Power Modulation . . . . .	566
3. Series Modulation . . . . .	567
4. Class B Modulation . . . . .	567
5. The Chireix System . . . . .	567
6. The Doherty System . . . . .	570
6.1. The Improved Doherty System . . . . .	574
6.1.1. Design of a Doherty Amplifier . . . . .	574
6.2. Grid-Modulated Amplifier . . . . .	576
6.2.1. Design of Grid-Modulated Doherty Amplifier . . . . .	577
6.2.2. Example of a Practical Circuit . . . . .	584
6.2.3. Representation of Voltages and Currents in the Grid-Modulated Doherty Amplifier . . . . .	589
7. The Fortescue System . . . . .	592
8. The Floating Carrier System . . . . .	593
9. Efficiencies of Output Stages of Different Systems . . . . .	595
9.1. Class A High-Power Modulation (includes Heising and Series Modulation) . . . . .	595
9.2. Class B High-Power Modulation . . . . .	596
9.3. Low-Power Modulation . . . . .	597
9.4. The Chireix System . . . . .	597
9.5. The Doherty System . . . . .	598
9.5.1. The Improved Doherty System . . . . .	599
9.6. The Fortescue System . . . . .	600
10. Comparison of Different Systems . . . . .	601
11. Observed Overall Efficiency of Transmitters . . . . .	603
12. H.T. Smoothing Circuits . . . . .	605
12.1. Class B System . . . . .	606

<b>XV Operation and Maintenance of Transmitters</b>	<b>611</b>
1. Starting Up a Transmitter . . . . .	611
1.1. Putting a New Valve into Service . . . . .	612
2. Shutting Down a Transmitter . . . . .	612
3. Shutting Down in Extreme Emergency . . . . .	613
4. Line-up of Transmitter for Modulation . . . . .	613
4.1. Old-Type Programme Meter . . . . .	613
4.2. Peak Programme Meter . . . . .	614
5. Running Adjustments . . . . .	614
6. Installation of Spare Valves . . . . .	614
7. Changing Wave . . . . .	615
8. Reducing Power Output of a Transmitter . . . . .	617
8.1. Reducing the Number of Valves . . . . .	618
8.2. Reducing Coupling . . . . .	619
8.3. Reduction of H.T. . . . .	620
9. Operation of Transmitters in Parallel on the Same Wavelength . . . . .	620
10. Prevention and Clearance of Faults . . . . .	622
10.1. Maintenance Routines on Valves . . . . .	622
10.2. Maintenance Routines on Transmitters . . . . .	622
10.3. Clearing Faults . . . . .	623
10.3.1. Fault Analysis . . . . .	623

CONTENTS

	PAGE
<b>XVI Feeders, Aerial-Coupling Circuits and Aerials</b>	<b>624</b>
1. The Behaviour of Feeders . . . . .	625
1.1. Characteristic Impedance = $Z_0$ . . . . .	628
1.2. Loop Inductance, Capacity per Unit Length and Characteristic Impedances of Three Types of Feeders . . . . .	628
1.3. Propagation Constant, Attenuation Constant and Phase Shift Constant. Relations between Voltages and Currents in Properly Terminated Feeder and Sending-End Voltages and Currents . . . . .	631
1.4. Relation between Wavelength $\lambda$ and Phase Constant $\alpha$ . . . . .	634
1.5. Phase Velocity of a Progressive Wave. Relations between Phase Velocity, Wavelength and Frequency . . . . .	634
1.6. Attenuation of Feeders . . . . .	635
1.7. Standing Waves . . . . .	636
1.7.1. Instantaneous Voltages in an Open-Circuited Line . . . . .	636
1.7.2. Instantaneous Currents in an Open-Circuited Line . . . . .	639
1.7.3. Instantaneous Voltages and Currents in a Short-Circuited Line . . . . .	639
1.7.4. Derivation of Formulae for Voltages and Currents in Open-Circuited Line and Sending-End Impedance . . . . .	640
1.7.5. Voltages and Currents in Short-Circuited Line and Sending-End Impedance . . . . .	641
1.8. Line terminated in an Impedance not equal to its Characteristic Impedance . . . . .	642
1.8.1. Determination of Ratio between Incident and Reflected Currents and Voltages . . . . .	642
1.8.2. Sending-End Impedance of Line of Characteristic Impedance $Z_0$ , terminated in an Impedance $Z$ . . . . .	643
1.9. Determination of Wavelength in a Feeder or Transmission Line . . . . .	645
1.10. Nodes and Antinodes in a line terminated in a Mismatched Load-Taking Power . . . . .	645
2. Circle Diagrams . . . . .	646
2.1. Method of Entering Parallel Represented Impedances . . . . .	648
3. Impedance Matching in Feeders . . . . .	652
3.1. Magnitude of Standing Waves . . . . .	652
3.1.1. Standing Wave Ratio . . . . .	653
3.1.2. Use of Circle Diagram to determine the Magnitude of the Standing Wave Ratio in a Feeder . . . . .	654
3.2. Determination of Terminal Impedance from the Currents at Nodes and Antinodes . . . . .	655
3.3. Impedance Matching in Short-Wave Feeders. Use of Tails for Impedance Matching . . . . .	655
3.4. Impedance Matching by Use of Inserted Length of Feeder of Different Impedance from the Main Feeder . . . . .	658
4. The Quarter-Wave Line . . . . .	662
5. Feeders as Filters . . . . .	664
5.1. The Tapped Quarter-Wave Line . . . . .	666
6. Conductor Sizes and Power-Carrying Capacity of Feeders . . . . .	667
7. Short-Wave Transmitting Aerials . . . . .	668

CONTENTS

XVI Feeders, Aerial Coupling Circuits and Aerials— <i>continued</i>	PAGE
7.I. Arrangement and Method of Designation of Short-Wave Arrays . . . . .	671
7.II. Performance of Arrays . . . . .	672
7.III. Power-Density Diagrams . . . . .	672
7.II2. Calibration of Power-Density Diagrams . . . . .	683
7.2. Slewing of Arrays . . . . .	684
7.3. Reflectors . . . . .	684
7.4. The Impedance Presented by a Half-Wave Dipole . . . . .	686
7.4I. Centre-Fed Dipole . . . . .	686
7.42. Shunt-Fed Dipole . . . . .	687
7.43. End-Fed Dipole . . . . .	687
7.5. Impedance of an Array . . . . .	688
7.6. Size of Conductor used in Dipole Arrays . . . . .	688
7.7. Kraus Aerial . . . . .	689
7.8. Lengths of Half-Wave Dipoles . . . . .	689
8. Impedance Matching in Medium and Long-Wave Feeders . . . . .	691
8.1. Essential Points to be observed in Adjustment of Aerial Circuits . . . . .	691
8.2. Aerial-Coupling Unit . . . . .	692
8.3. Equivalence of Series and Parallel Impedances . . . . .	693
8.4. L Networks for Use as Impedance Transforming Sections . . . . .	694
8.5. Method of Setting Up Aerial Coupling Circuits . . . . .	696
8.5I. Choice of Form of Circuit on Secondary Side of the Coupling Unit . . . . .	698
8.6. Matching of Low Impedances . . . . .	700
9. Insertion of Rejector Circuits for the Prevention of "Throw-in" . . . . .	701
10. Operation of Two Transmitters on Different Wave-lengths into a Single Aerial . . . . .	705
11. Losses in Aerial Tuning Huts . . . . .	705
12. Impedance Matching in Long-Wave Aerial Circuits . . . . .	706
12.1. Principles of Design in Long-Wave Aerial Circuits of B.B.C. Transmitter at Droitwich . . . . .	711
12.II. Simulation of Reactance Curve by Series Resonant Circuit . . . . .	712
12.I2. Neutralization of Aerial Reactance . . . . .	713
12.I3. Power Factor Correction at Two Sideband Frequencies . . . . .	714
12.I4. Calculation of Circuit Impedances . . . . .	716
12.I5. Frequency Response . . . . .	722
12.I6. Analysis of Circuit used at Droitwich and Method of Design of Component Networks to Build up Overall Required Phase Shift . . . . .	723
13. Relations between Inductance and Capacity per Metre, Characteristic Impedance and Phase Velocity . . . . .	727
13.1. Inductance of Straight Vertical Wire . . . . .	728
13.2. Value of Condenser required to Neutralize Reactance of Grid Lead . . . . .	729
13.3. Elimination of Phase Shift in Grid Lead . . . . .	731
13.4. Neutralization of Reactance of Earth Lead . . . . .	733
14. Stress Diagrams in Aerial Arrays . . . . .	734

CONTENTS

XVI Feeders, Aerial Coupling Circuits and Aerials— <i>continued</i>	PAGE
14.1. Vector Conventions . . . . .	735
14.2. Force and Space Diagrams . . . . .	736
14.3. Bow's Notation . . . . .	737
14.4. Catenary . . . . .	737
14.5. Triatic with Single Load . . . . .	740
14.6. Multi-loaded Triatic . . . . .	743
14.7. Curtain Array . . . . .	746
14.8. Windage and Ice . . . . .	749
14.9. Factors of Safety . . . . .	750
<b>Index</b> . . . . .	<b>753</b>